

EE 5193 FPGA and Verilog HDL

**Assignment 1**


Due on 11th June, by 6.00 PM

1. a. Minimize the four-variable logic function using Karnaugh map and realize it with NAND gates.

$$f(A,B,C,D) = \sum m(0,1,2,3,5,7,8,9,11,15)$$

		AB				
		00	01	11	10	
CD	00	1	0	0	1	
	01	1	1	0	1	
	11	1	1	1	1	
	10	1	0	0	0	

$$F = B'C' + A'B' + A'D + CD$$

 

- b. Minimize the logic function in POS form.

$$F' = (BD' + ABC' + ACD')'$$

$$F = (B' + D)(A' + B' + C)(A' + C' + D)$$

2. Design a Gray-to-Decimal code converter using 8:1 multiplexers and NAND gates.

	Gray		Code		Decimal				
	g3	g2	g1	g0	d3	d2	d1	d0	
0	0	0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	0	1	1
3	0	0	1	1	0	0	1	0	2
2	0	0	1	0	0	0	1	1	3
6	0	1	1	0	0	1	0	0	4
7	1	1	1	0	0	1	0	1	5
5	0	1	0	1	0	1	1	0	6
4	0	1	0	0	0	1	1	1	7
12	1	1	0	0	1	0	0	0	8
13	1	1	0	1	1	0	0	1	9


$D3 = \Sigma m(12, 13)$

$D2 = \Sigma m(4, 5, 6, 7)$


$D1 = \Sigma m(2, 3, 4, 5)$

$D0 = \Sigma m(1, 2, 4, 7, 13)$


d3	000		001		010		011		100		101		110		111	
g3' (0)	0	1	2	3	4	5	6	7								
g3 (1)	8	9	10	11	12	13	14	15								
	I0	I1	I2	I3	I4	I5	I6	I7								

 


d2				g2g1g0				
	000	001	010	011	100	101	110	111
g3' (0)	0	1	2	3	4	5	6	7
g3 (1)	8	9	10	11	12	13	14	15
	I0	I1	I2	I3	I4	I5	I6	I7

 

d1				g2g1g0				
	000	001	010	011	100	101	110	111
g3' (0)	0	1	2	3	4	5	6	7
g3 (1)	8	9	10	11	12	13	14	15
	I0	I1	I2	I3	I4	I5	I6	I7

 


d0				g2g1g0				
	000	001	010	011	100	101	110	111
g3' (0)	0	1	2	3	4	5	6	7
g3 (1)	8	9	10	11	12	13	14	15
	I0	I1	I2	I3	I4	I5	I6	I7

 

3. Consider the following circuit where the propagation delay of logic gates in the circuit are:

NOT=10ns, AND=20ns, OR=20ns.

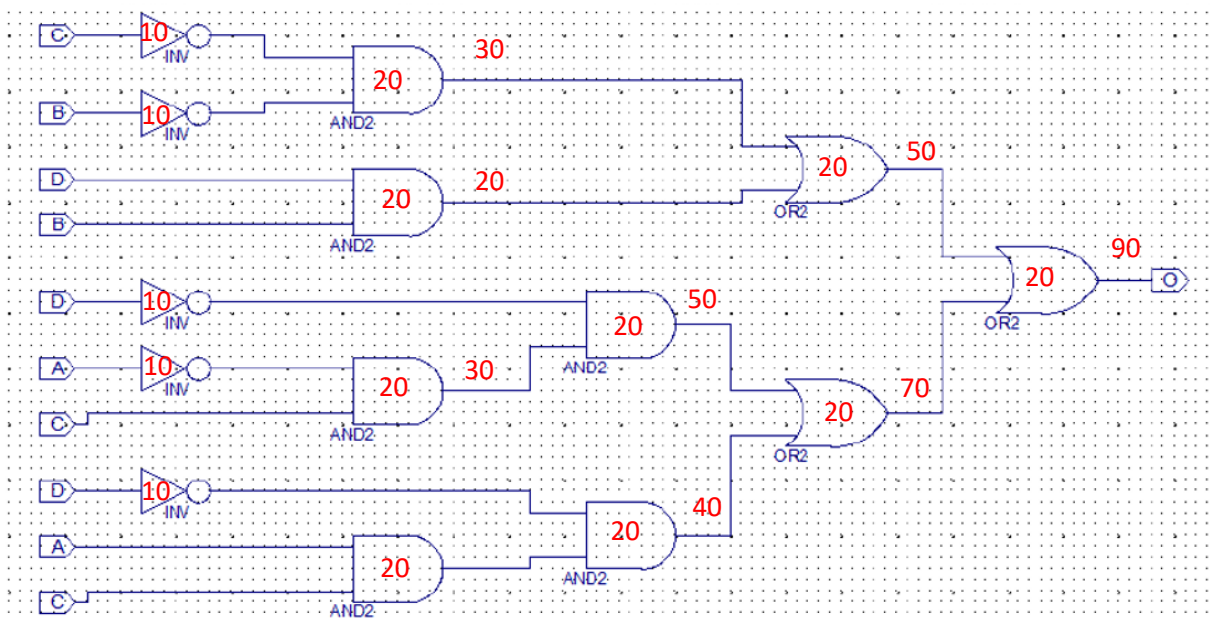

a. Draw a truth table for the given circuit. Draw a Karnaugh map using the truth table and derive a sum of product (SOP) expression for the results.

		AB			
CD		00	01	11	10
	00	1	0	0	1
	01	1	1	1	1
	11	0	1	1	0
	10	1	0	1	1

$$F = C'D + BD + B'D' + ABC$$

b. Describe advantages and disadvantages of your SOP expression vs the given circuit.

There are unaccounted hazards in my circuit. Advantage is that the circuit is minimized.

c. If the given circuit is used as combinational logic within a clocked system, what is the maximum clock speed of the system? Will the maximum clock speed change if circuit of the SOP expression is used instead?

Max clock speed is 90ns. 50ns with SOP circuit, the max clock speed changes.